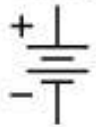





Battery



Wire



Resistor

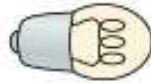


Bulb



Junction




Capacitor

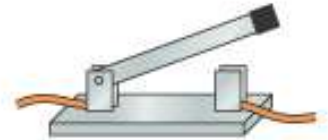

Switch




Batteries

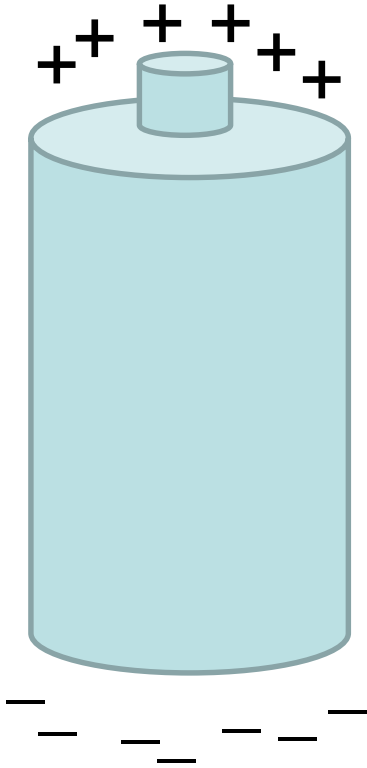


- Use chemical energy to maintain a charge separation
- Voltage or potential difference
- $V = E/q$, constant
- Unit is the Volt (V)


Current

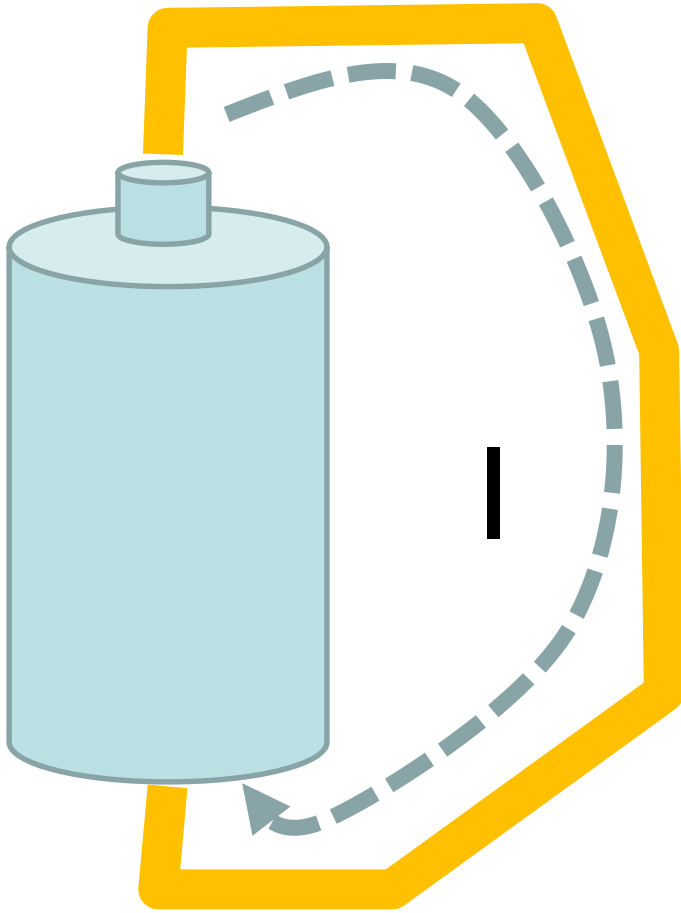

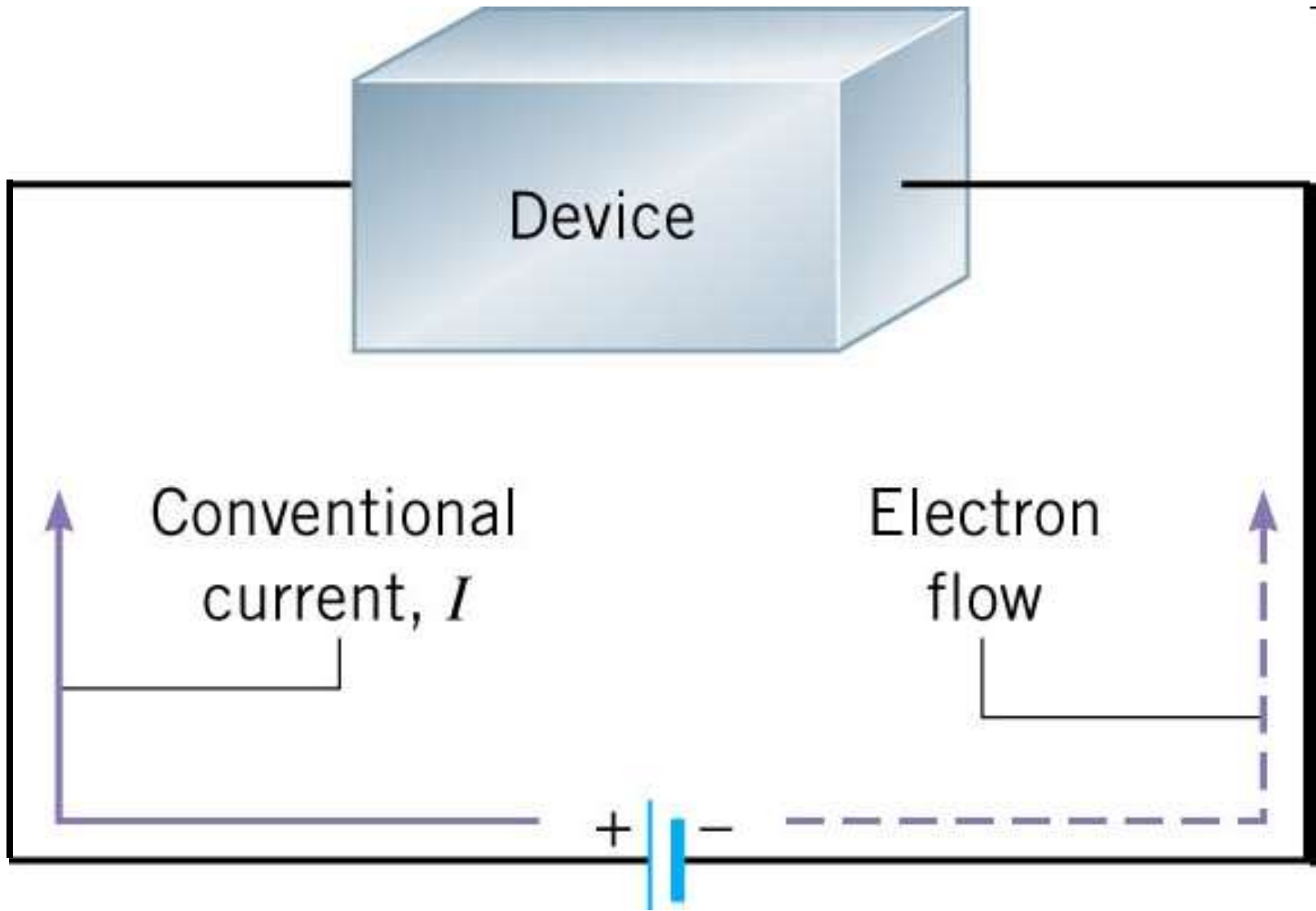- Air is an insulator
- Connect a conductor from + to -, have a circuit
- Charge flows
- Chem E used up keeping charge separation
- Current $I = q/t$
- Unit is Amperes (A)



Resistor

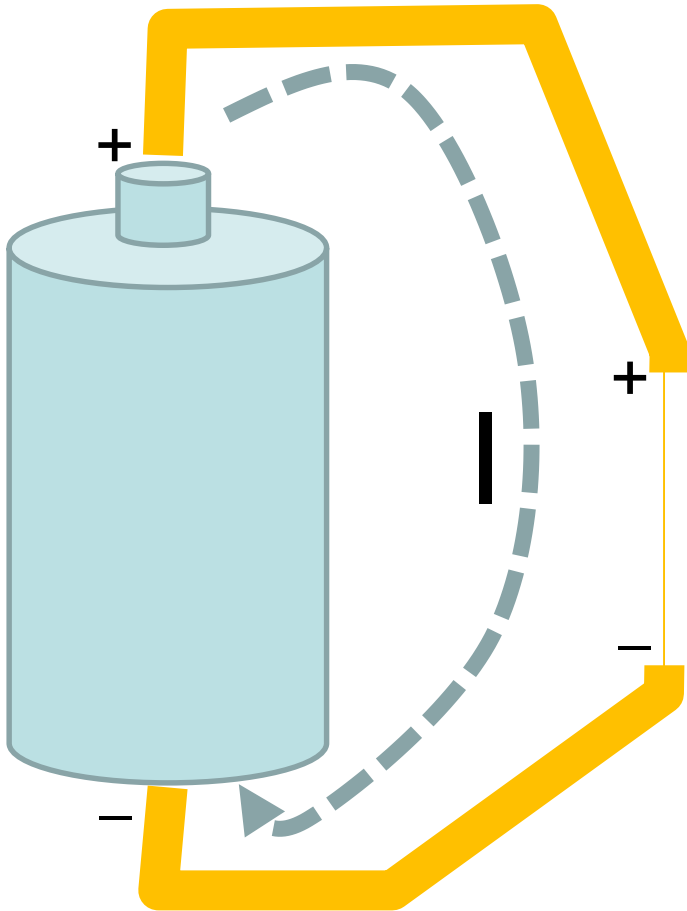

- Very thin conductor
- Restricts current flow
- Thinner means higher resistance
- Creates a traffic jam.
- Result is a charge separation or voltage V_R across resistor in a circuit.

Power

- Power, $P = E / t$ (watts)


- Simple math trick

$$P = E/q \times q/t = VI$$

- Battery supplies power and drives current
- Resistor dissipates power as heat “Joule Heating”
- Energy is conserved

$$\therefore P_{in} = P_{out}$$

$$V_B I = V_R I \rightarrow V_B = V_R$$

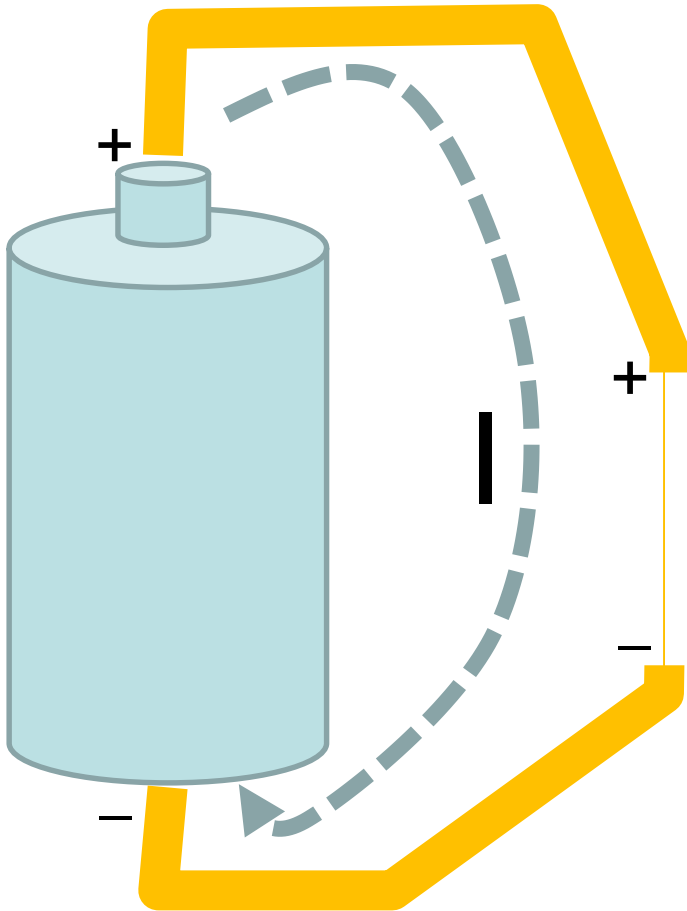

Ohm's Law

- For conductors, define resistance


$$R = \frac{V_R}{I} \quad \text{unit is } \Omega \text{ (Ohm)}$$

- For certain conductors (the type we make resistors out of), R is constant

Battery-Resistor Circuit




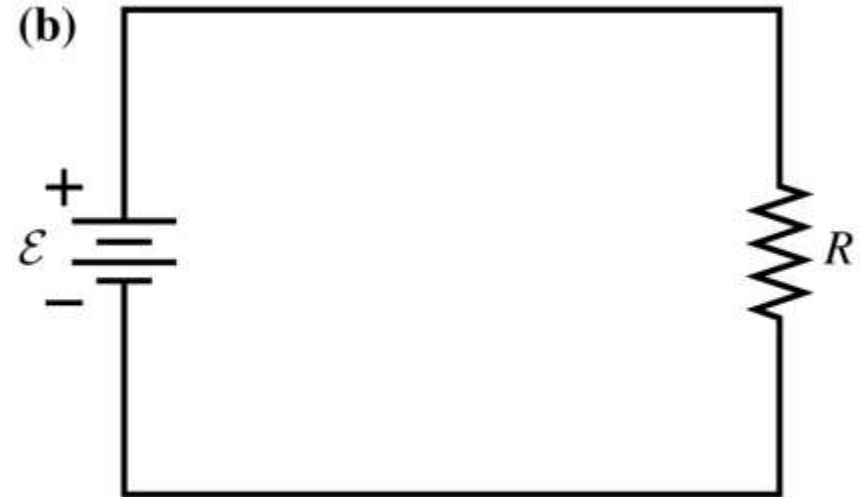Copyright © 2004 Pearson Education, Inc., publishing as Addison Wesley



Copyright © 2004 Pearson Education, Inc., publishing as Addison Wesley

Simulation

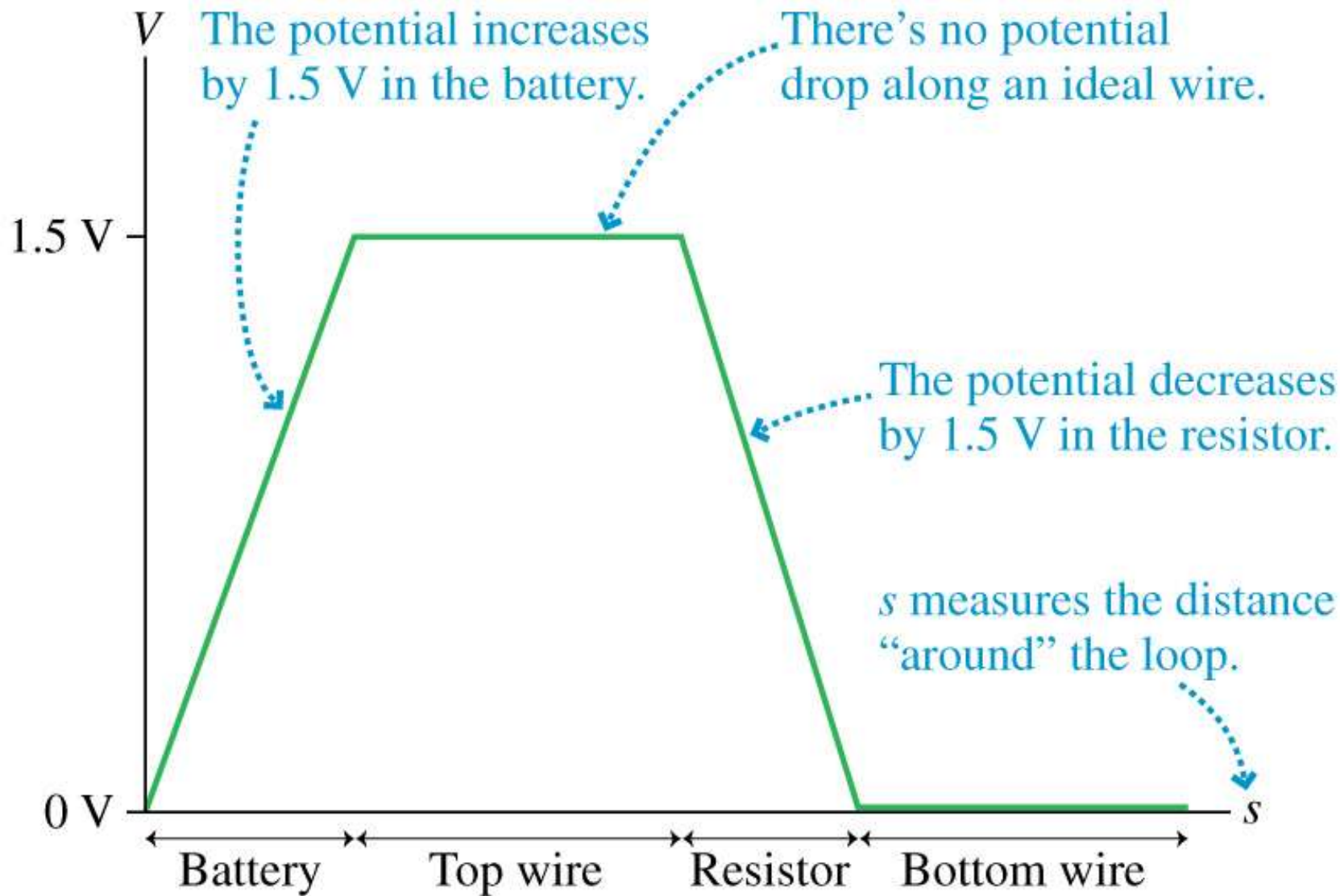

Goal

- Analyze circuit with many resistors
- Find nodes/junction where three or more wires come together
- Identify branches, paths from one node to the next
- Identify common nodes – connected by a bare wire (no resistor)
- Use $P_{in} = P_{out}$
- Use $I_{in} = I_{out}$
- Use $V = IR$, Ohm's Law

